



جامعة الأمير مقرن بن عبد العزيز
University of Prince Mugrin

Electronics 1 Project

Presenters:

Mustafa Haider
Id: 4010177

Marwan Baitar
Id: 4110259

Abdulsalam Kanjou
Id: 4110002

Course Title

EE222-Electronics 1

Instructor

Dr. Mohammed Al Molla

Date

25/5/2022

Content


1	Introduction
2	Task 1/ Full Bridge Rectifier
3	Task 2/ Touch Sensor Circuit
4	Task 3/ Comparator Circuit
5	Task 4/ Testing different loads
6	Parameters Calculations
7	Limitation
8	Challenges
9	Work distribution
10	Conclusion



Introduction



- **Applying the gained knowledge**
- **Achieving the objectives:**
 1. **Designing a circuit based on requirements.**
 2. **Incorporating only (Electronics 1) materials.**
 3. **Simulation and data acquisition.**


Tasks	Topic
Task 1	Diodes.
Task 2	Online research and electrical circuit background.
Task 3	BJTs.
Task 4	

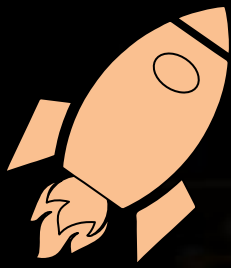

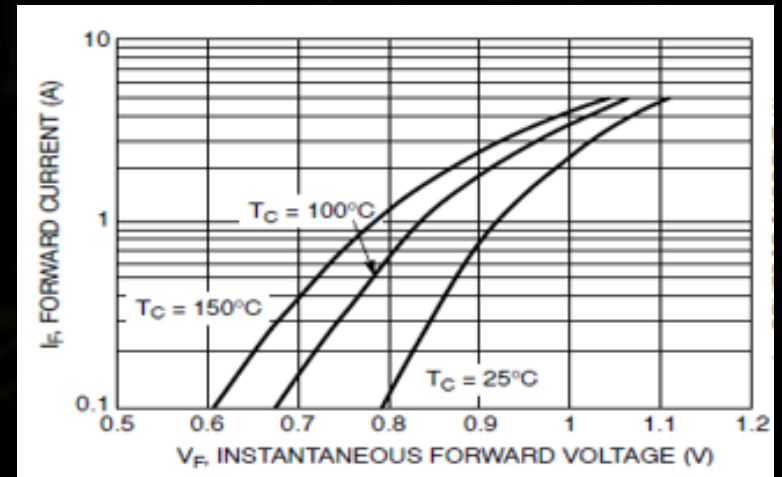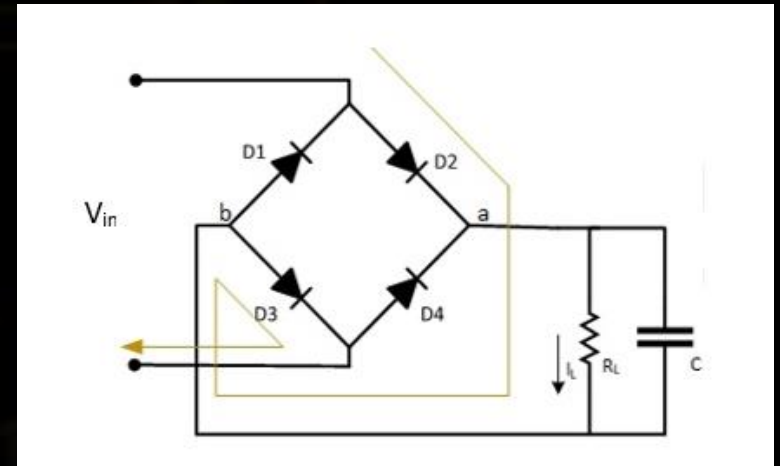Task 1 / Full Bridge Rectifier


- Converting AC to DC.
- The positive half-wave & the negative half-wave Cycle.
- Diode characteristics.



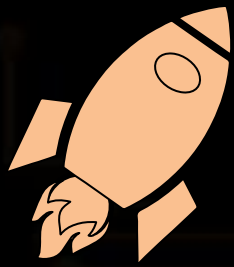


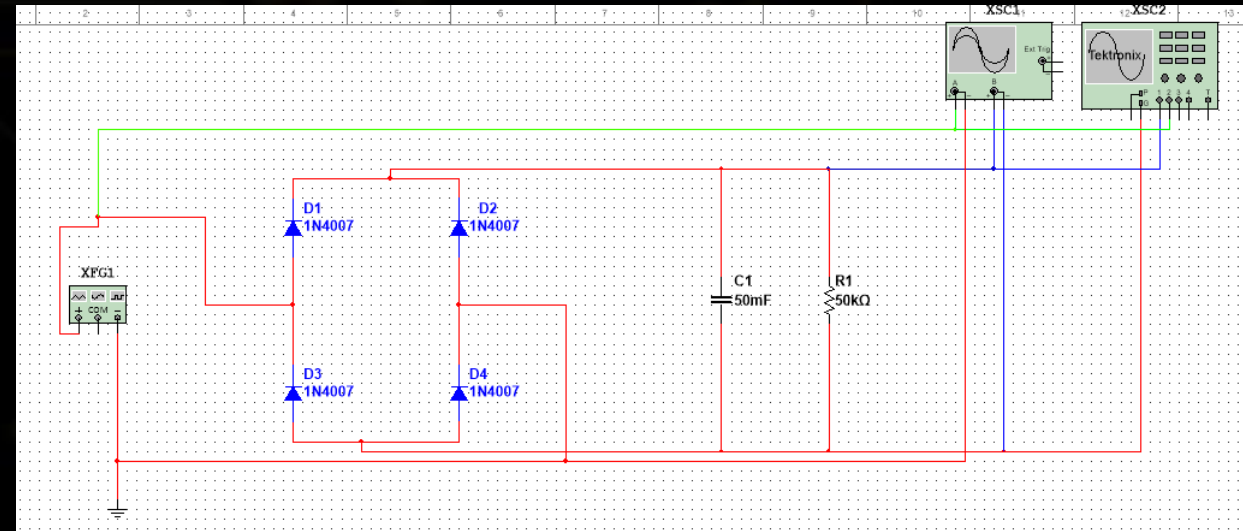Task 1/ SIMULATION

$$V_{r(pp)} = \left(\frac{1}{fR_L C} \right) V_{p(rect)}$$




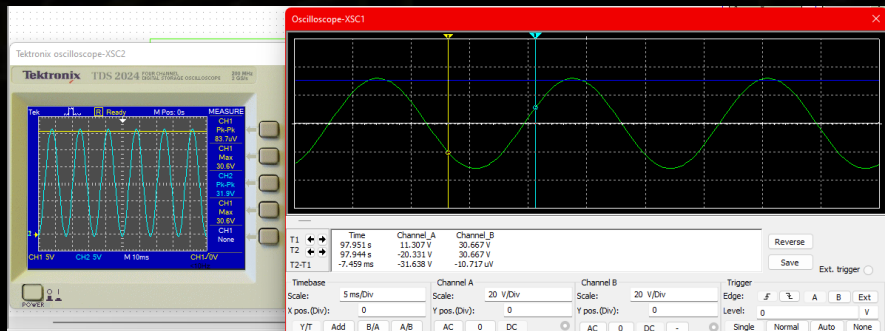The simulation of the bridge rectifier circuit



The minimal output Ripple Voltage (DC Voltage)

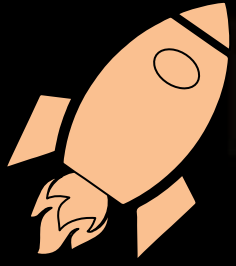The peak-peak ripple voltage was found 83.7uV



Task 2 / Touch Sensor Circuit


- **Difficulties:**

- 1- Amperes = Less than 1 mA, Less than 10 mA


- 2- $1\text{k Ohm} < \text{Human resistor} < 10\text{k Ohm}$.

- **Mechanism:**

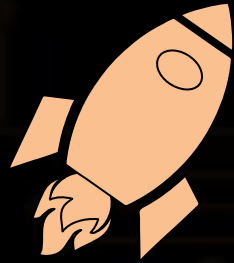
- Switch + Resistor + Effects of the Comparator Circuit



Task 2 / Simulation

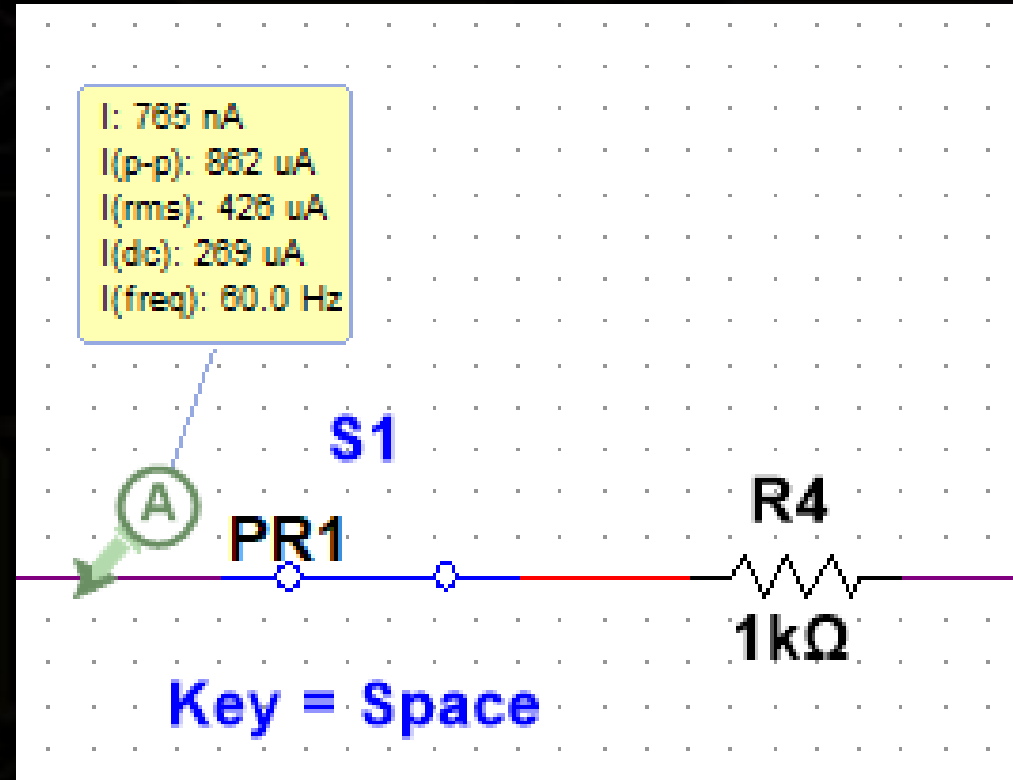

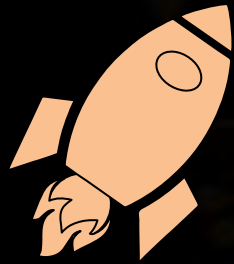Simulation + Representation of the Touch Sensor



Task 3 / Comparator Circuit

- **NPN BJT used.**


Symbol	Parameter	Value		Unit
		BD235	BD237	
V_{CBO}	Collector-base voltage ($I_E = 0$)	60	100	V
V_{CER}	Collector-emitter voltage ($R_{BE} = 1\text{ k}\Omega$)	60	100	V
V_{CEO}	Collector-emitter voltage ($I_B = 0$)	60	80	V
V_{EBO}	Emitter-base voltage ($I_C = 0$)	5		V
I_C	Collector current	2		A
I_{CM}	Collector peak current ($t_p < \text{ms}$)	6		A
P_{TOT}	Total dissipation at $T_{\text{case}} = 25^\circ\text{C}$	25		W
T_{stg}	Storage temperature	-65 to 150		$^\circ\text{C}$
T_J	Max. operating junction temperature	150		$^\circ\text{C}$

Absolute maximum ratings

IB

IC


VCE

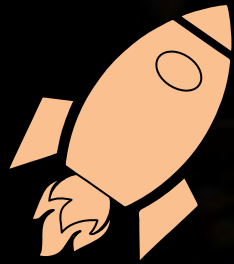


Task 3 / Comparator Circuit

Symbol	Parameter	Test conditions	Min.	Typ.	Max.	Unit
I_{CBO}	Collector cut-off current ($I_E = 0$)	$V_{CB} = \text{rated } V_{CBO}$ $V_{CB} = \text{rated } V_{CBO} \quad T_C = 150^\circ\text{C}$		-	0.1 2	mA mA
I_{EBO}	Emitter cut-off current ($I_C = 0$)	$V_{EB} = 5V$		-	1	mA
$V_{CEO(sus)}^{(1)}$	Collector-emitter sustaining voltage ($I_B = 0$)	$I_C = 100\text{mA}$ for BD235 for BD237	60 80	-		V V
$V_{CE(sat)}^{(1)}$	Collector-emitter saturation voltage	$I_C = 1A$ $I_B = 0.1A$		-	0.6	V
$V_{BE(on)}^{(1)}$	Base-emitter on voltage	$I_C = 1A$ $V_{CE} = 2V$		-	1.3	V
$h_{FE}^{(1)}$	DC current gain	$I_C = 150\text{mA}$ $V_{CE} = 2V$ $I_C = 1A$ $V_{CE} = 2V$	40 25	-		


Electrical characteristics

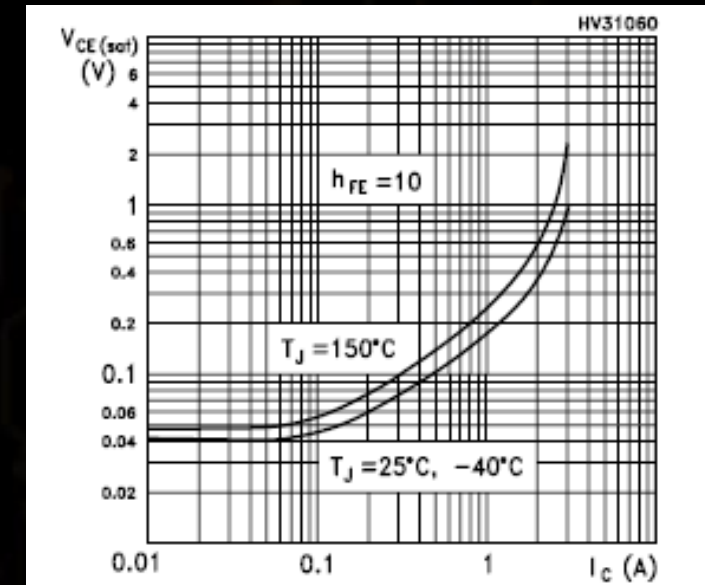


BJT characteristic curve

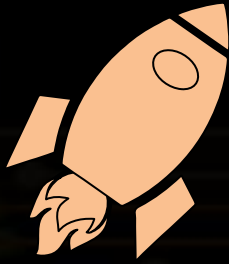

Task 3 / Simulation

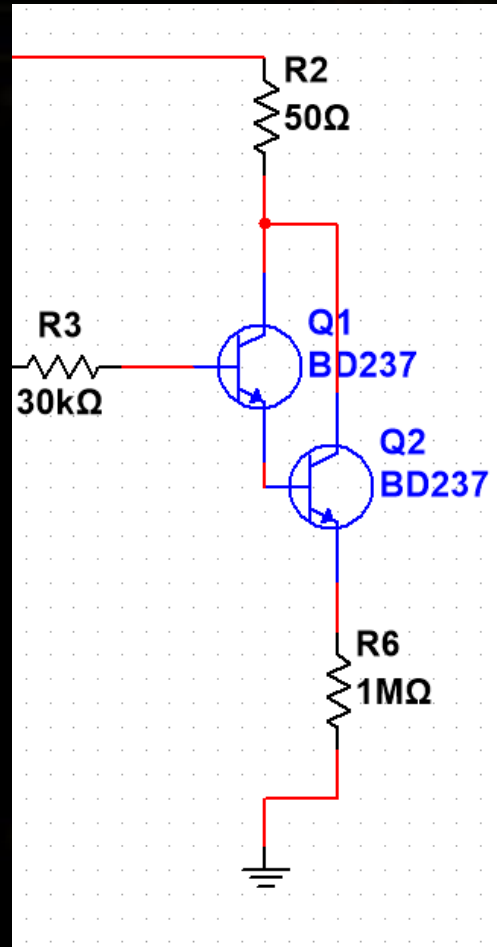

Comparator Circuit Simulation

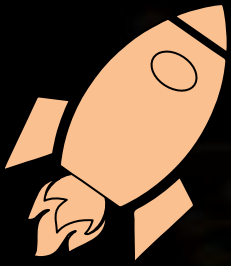


Task 4 / Testing different loads


- We needed to make sure that the circuit works with different loads. Such as:
 - Different colored LEDs.
 - Lasers.
 - Buzzers.
- The circuit must operate these loads while keeping the current through the touch sensor low.



Task 4 / Simulation

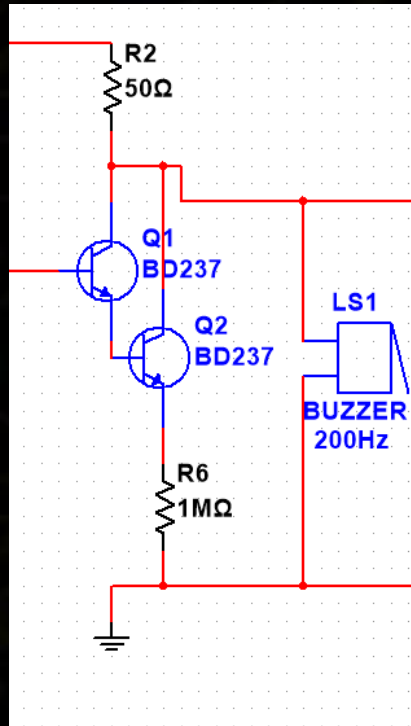

The Buzzer Connected to the Circuit

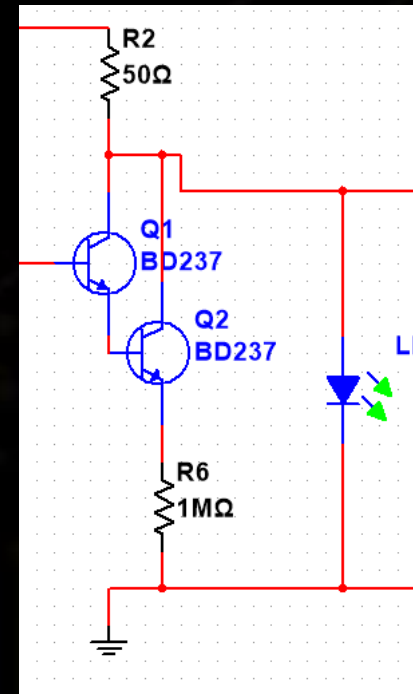

LED Connected to the Circuit




Parameters Calculations

- the most important parameters are:

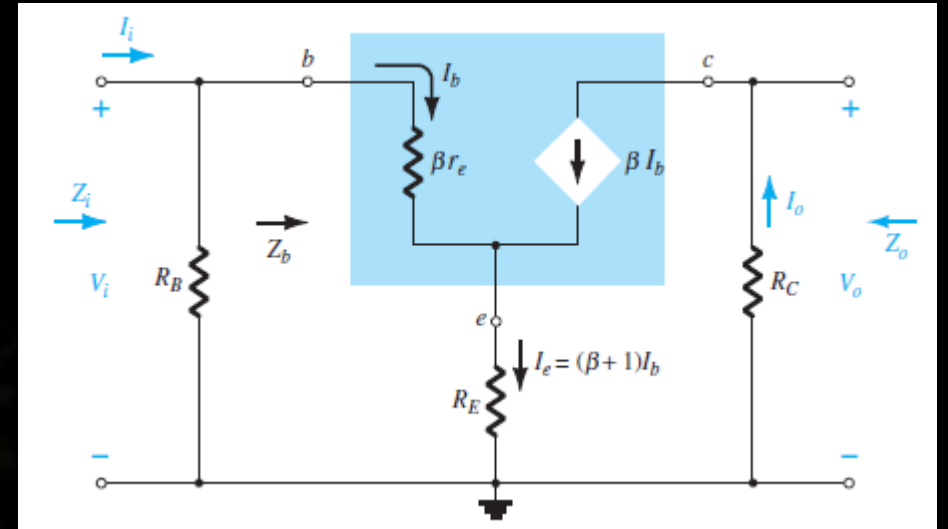1. Z_i : input impedance.
2. Z_o : output impedance.
3. I_i : current entering the Base.
4. I_o : current entering the Collector.

- We can find some variables first:

- r_{e1} & r_{e2} (reverse emitter resistors): $r_{e1} = r_{e2} = 25\text{mV} / I_e = 25\text{m} / 111\mu = 225\text{ Ohm}$.
- Beta: $I_C / I_B = 153$
- Z_b (I_B path impedance) = $\text{Beta} * R_E = 153\text{M Ohm}$





Parameters Calculations


- So, our parameters will be:

1- $Z_i = Z_b // R_B = 29994 \text{ Ohm}$

2- $Z_o = R_C = 50 \text{ Ohm}$

3- $I_i = 458 \text{ nA}$

4- $I_o = 70.1 \text{ uA}$

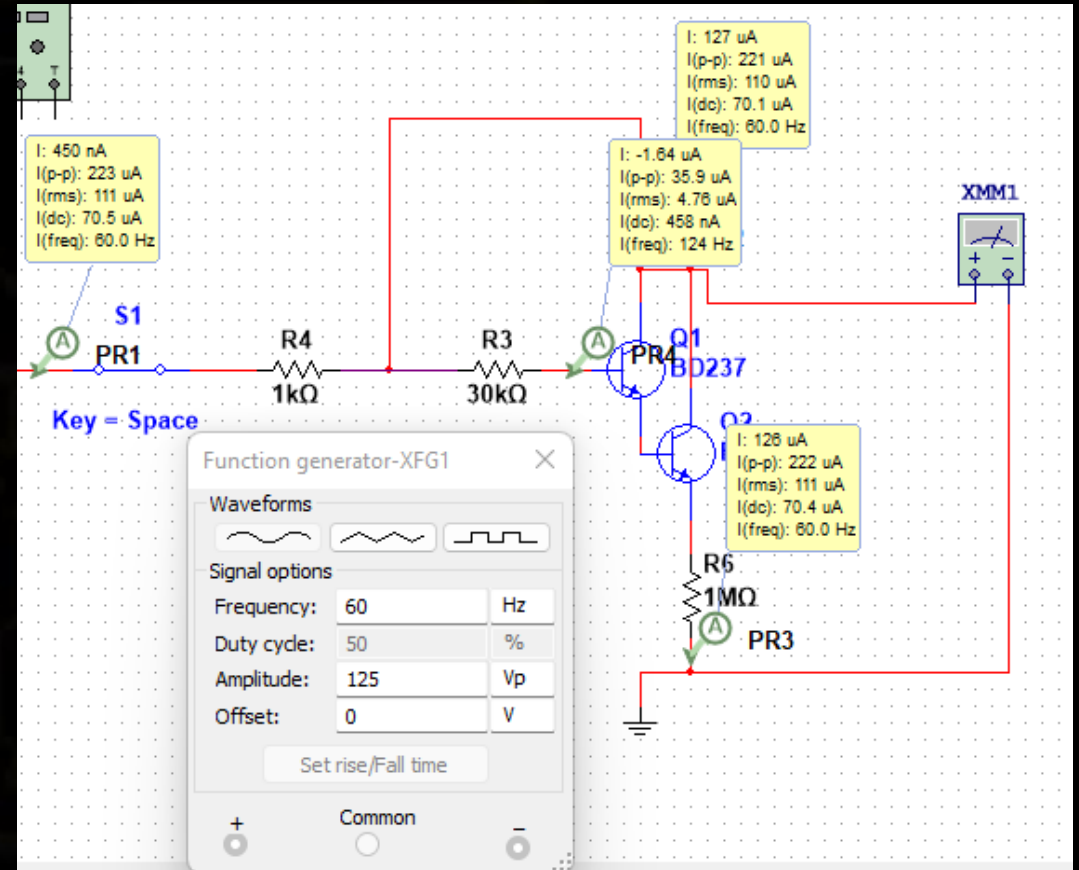

- And the final important parameter is the gain $A_V = -R_C/R_E = -50$



Limitation

- Our circuit was limited between 125 and 311 V_{peak} - AC.
 - Below 125V_p, the buzzer will stop working.
 - Above 311V_p, the current through the touch sensor will cause a shock to the person touching it.



Challenges

- **Challenges:**

- 1) Multiple error in Multisim**

- 2) Miscalculations**

- 3) Finding proper current through the human hand**

- 4) Having suitable voltage for output**



Work distribution

- **Work distribution:**

- 1. Mustafa = Task 1 + Simulation 1 + written content + ppt design**
- 2. Marwan = Task 2 + Task 3 + Simulation 2 + written content + ppt content**
- 3. Abdulsalam = Task 4 + Simulation 3 + written content + ppt content**

NOTE: there was an overlap between the members in the work.



Conclusion

**3 Working
Circuits**

**4 Tasks
Done**

- **Seeking improvements in the future**



References

- BD237 Data-sheet, STMicroelectronics.
- Electrical Engineering Department, University of Prince Mugrin (UPM). Laboratory Manual for Electronic Circuits 1.
- Nashelsky, L., & Boylestad, R. L. (2021). Electronic Devices and Circuit Theory Eleventh Edition.
- *Resistance of Humans*. (2021). Fundamentals of Electricity.
<https://c03.apogee.net/mvc/home/hes/land/el?utilityname=citizenselectric&spc=foe&id=4657#:~:text=Human%20resistance%20is%20about%2010%2C000,or%20impedance%20to%20current%20flow>
- 1N4007 Data-sheet, Onsemi.

Thank You

